

CMOS Front-End for Micropower RF Wireless System

**R. Rofougaran, I. Bhatti, T.H. Lin,
F. Newberg, W.J. Kaiser
UCLA Electrical Engineering**


Outline


- Introduction to Wireless Integrated Network Sensors (WINS) Project: Network, Applications, Nodes
- Unique Transceiver Requirements
- RF Architecture:
 - **Receiver:** Preselector, LNA , Mixer, VCO and PLL Architecture
 - **Transmitter:** PA Architecture
- Future work: (WINS integration)
- Summary

Wireless Integrated Network Sensors (WINS)


- Low-power Networking

Medical instrument
internetworking




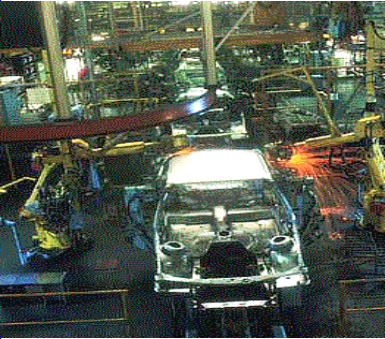

Industrial controls



Consumer

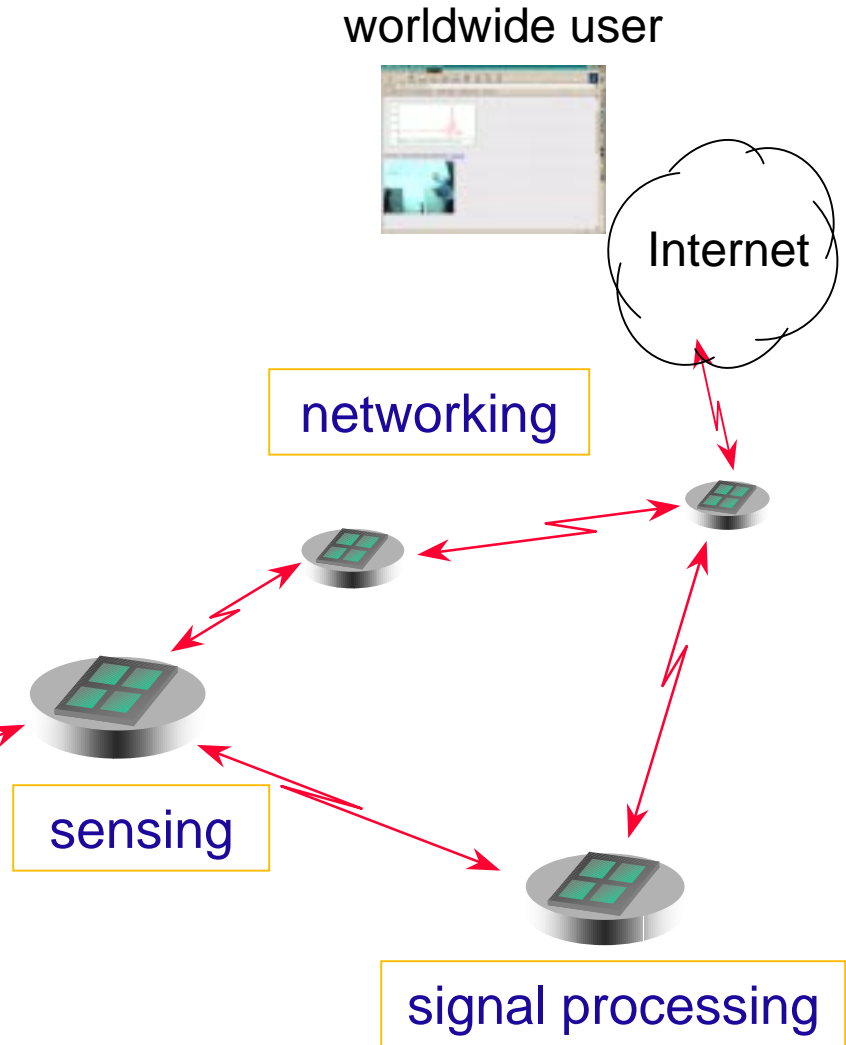

Network Characteristics

- Dense node distribution
- Short range (<30m)
- Low bit rate (<100kbps)
typical sensors systems are band limited
- Latency tolerant
- Compact cell
- 3 years life
- 100 μ W average
- 3mW peak


Implement multihop for power reasons:

RF path loss:

$$P \propto \frac{1}{R^\alpha} \quad (\alpha \approx 3-5)$$

Relative system power advantage for N-hop chain:
 
$$\frac{P_{total}(N)}{P_{total}(1)} \propto \frac{1}{N^{(\alpha-1)}}$$



WINS Communication Requirements

- In the design of WINS communication system must consider:
 - Stringent power limitation \Rightarrow low power architecture
 - wireless microsensor applications \Rightarrow reduced data rate
 - Multihop network operation \Rightarrow node-to-node link budget is relaxed



	Specs	Extension
Operation frequency	ISM band (902-928 MHz)	2.4 GHz
Modulation scheme	binary FSK	4-FSK
Channel spacing	500 kHz	250 ~ 500 kHz
Tone frequency	100 kHz	60 ~ 100 kHz
Data rate	10 kbps	1 ~ 100 kbps
Frequency Accuracy	20 ppm	< 30 ppm
Transmission power	-10 ~ 10 dBm	nominal: 0 dBm
SNR required	< 10 dB (BER: 10e-3)	TBD
Hopping rate	100 hops/sec	TBD

WINS Communication Approaches





- Signaling: FSK
 - allow power-efficient non-linear PA
 - allow low power modulation and demodulation circuitry
 - spectrum efficiency is not a main concern in most microsensor applications
- FSK Tone Frequency: 100kHz
 - To minimize the impact of baseband $1/f$ noise and account for the inaccuracy of reference frequency source (20 ppm), the FSK tone frequency is chosen to be 100 kHz, independent of data rate.
- Channel Spacing: 250-500kHz
 - 250 ~ 500 kHz; lower bound is set by the baseband channel-select filter design (avoid sharp transition from passband to stopband), upper bound is set by FCC regulation (at least 50 hopping channels are required)
- Path Loss:
 - assume $n=4$, $d=30$ m \Rightarrow maximum path loss ~ 92 dB
- Sensitivity (MDS, desired minimum detectable signal):
 - MDS = 10 dBm (maximum transmitting power) -92 dB (path loss) = -82 dBm

WINS Communication Approaches

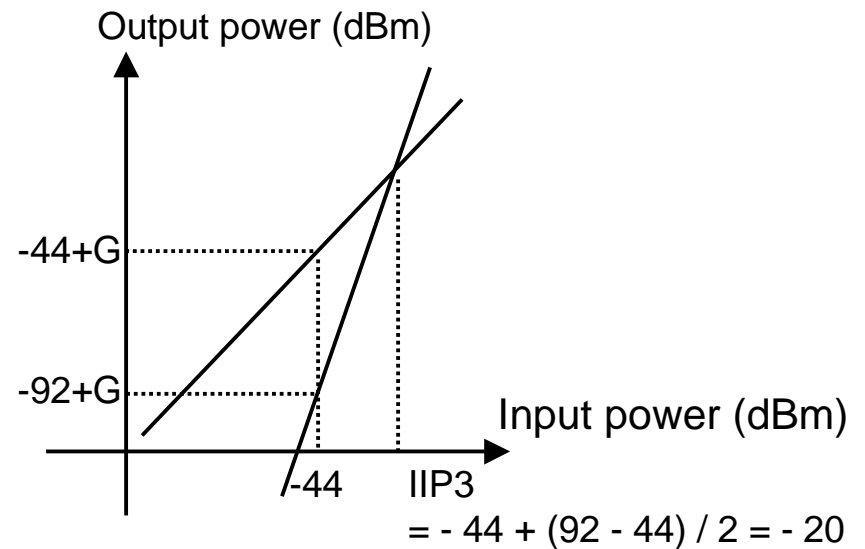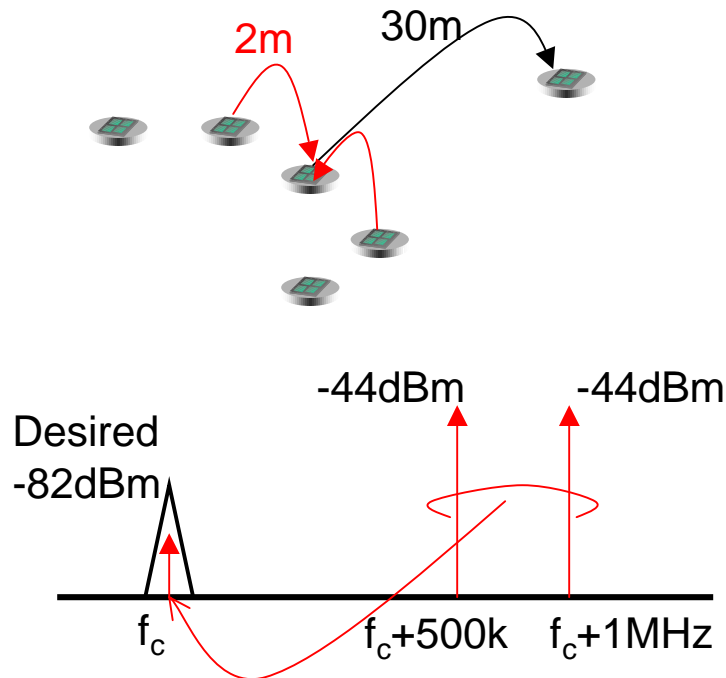- Noise Figure:
 - $NF = 174 - 10 \times \log_{10} BW - SNR_{min} + MDS - 5 \text{ dB (margin)} = 25 \text{ dB}$
- Linearity (IIP3):
 - With simple power control scheme and proper nodes distribution, the two-tone interfere is at -44 dBm; the IIP3 is calculated to be -16 dBm (with 4dB margin).
 - 2nd-order distortion (IP2) is mitigated by differential circuit architectures



WINS Nodes

    

- WINS RF Modem
- Network Interface
- Memory
- Microcontroller
- State Machine
- DSP
- ADC
- Sensor Interface
- Sensors



WINS vs. Existing Wireless System

Characteristic	Wireless LAN	Cellular Telephony	WINS
Range	~ 200m	~ 5km	$\leq 30\text{m}$
Data Throughput	~ 2-10Mbps	~ 10kbps	$\leq 100\text{kbps}$

Conclusions:

- Range and bandwidth reduction : ***60 - 80dB gain in link budget***


Why Design a New Receiver?

- Performance specifications of receivers:

	Cellular	Bluetooth	WINS
Noise Figure	8dB	Est (- 26)	~ 25dB
Sensitivity	-102dBm	-70dBm	~ -80dBm
Data rate	~10 kbps	1Mbps	≤ 100kbps
Current consumption	35 - 40mA	≤ 20mA	~ 1 mA

- Challenge:** Minimum noise figure and best sensitivity for long range communications.
- Specifications of the front-end receiver for WINS project:
 - Digital CMOS transistor
 - Current consumption ≤ 200 μ A
 - Gain \cong 20 - 25dB
 - Noise figure \cong 20 dB
- Challenge:** Micro power for short range communications (30 m)

Two Examined Receiver Architectures

 

Goal: 1mA entire receiver system peak current drain


- High-Q inductive loads
- Off chip integration: LTCC components

Two receiver architecture has been developed :

- ◆ Multi stage architecture: Preselector /LNA/Mixer
- ◆ Single stage architecture: Preselector/Combined LNA and Mixer

Two Architectures


1 0.8 μ technology

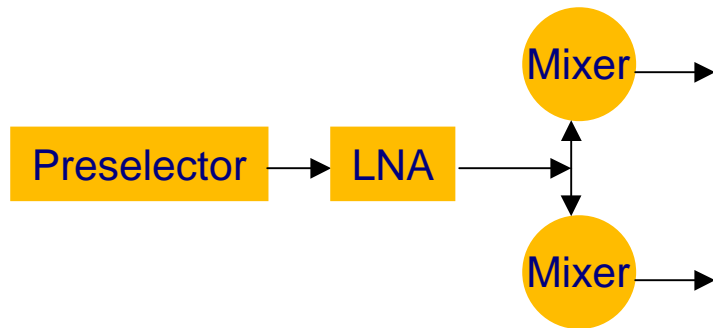

Multi stage: Gain achieved by

- **Preselector:** High Q elements
- **LNA transistors g_m :** Small due to the small current and relatively small transistor sizes
- **LNA output Impedance:** High Q components to generate large impedance at the output
- **Mixer input:** High impedance

2 0.6 μ technology

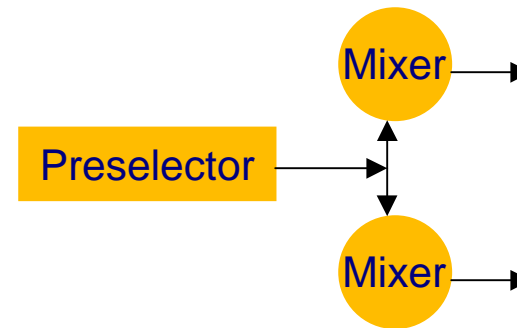


Single stage: Gain achieved by

- **Preselector:** High Q elements
- **Mixer transistors g_m :** Small due to the small current and relatively small transistor sizes
- **Mixer output Impedance:** High impedance

Mixer is the only current user stage! \Rightarrow Gain and less NF

Preselectors

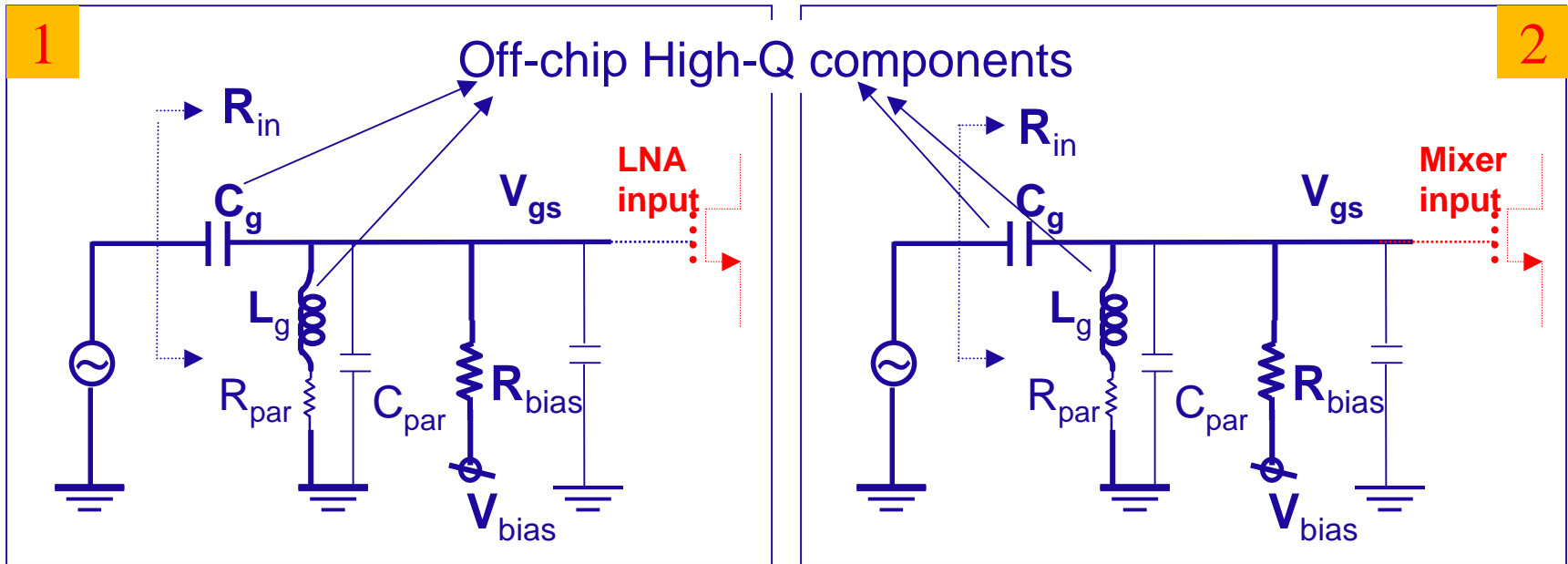

•Filtering

•Matching Choose L and C

input impedance at ω_{res} :

•Gain from V_s to V_{gs} :

$$\omega_{res} = R / \sqrt{L((C_g + C_{total}) R^2 - L)}$$


$$R \rightarrow \infty \quad \omega_{res} \approx 1 / \sqrt{L(C_g + C_{total})}$$

$$R_{in} \approx L / R_{bias} (C_g || C_{total})$$

$$V_{gs} / V_s \approx R \sqrt{(C_g || C_{total}) / L} \quad \text{Passive}$$

Half Circuits

1

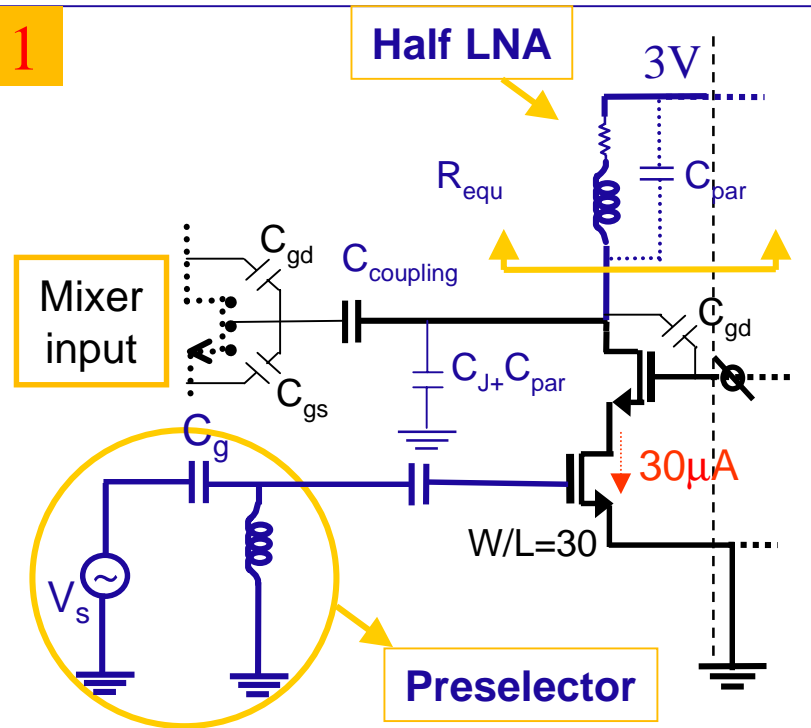


- LNA output impedance at ω_{res} :

$$R_{equ} = L / RC_{total}$$

Total gain:

$$A_v = g_m \cdot R_{equ} \cdot A_{preselector}$$

2

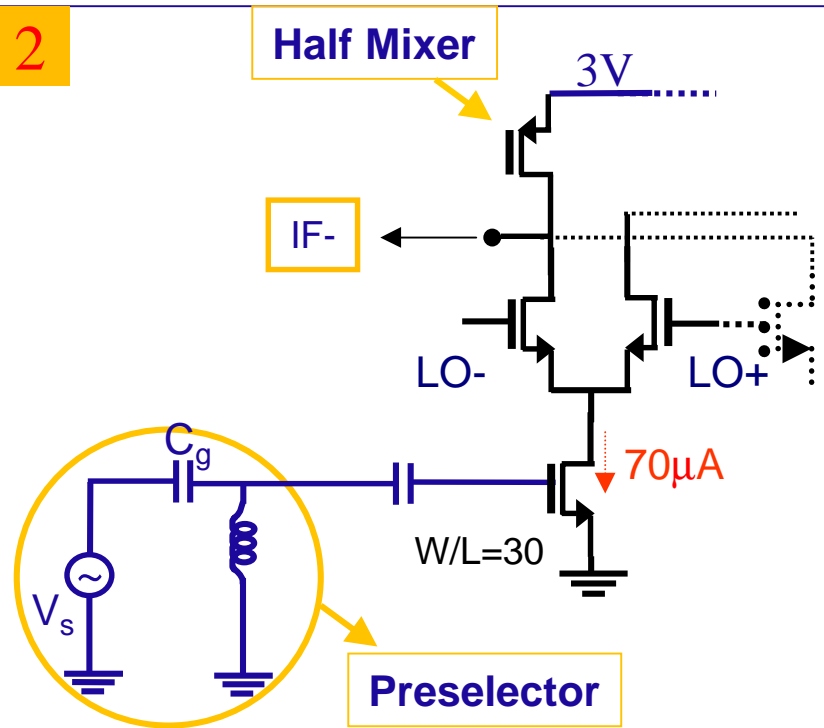


- High output impedance: Using active loads

Total gain:


$$A_v = g_m \cdot R_{equ} \cdot A_{preselector}$$

Mixers

 - Double-balanced Gilbert cell
- Direct conversion
- High output impedance
- Output bandwidth > 100 kHz




- Current consumption = 50 μ A

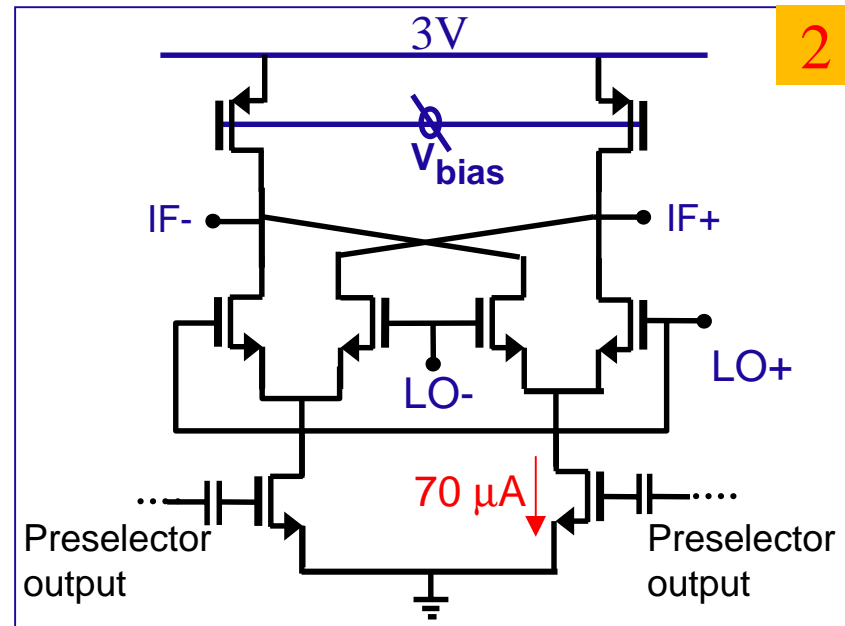


- Current consumption = 140 μ A

Layout and picture of the Front-end boards

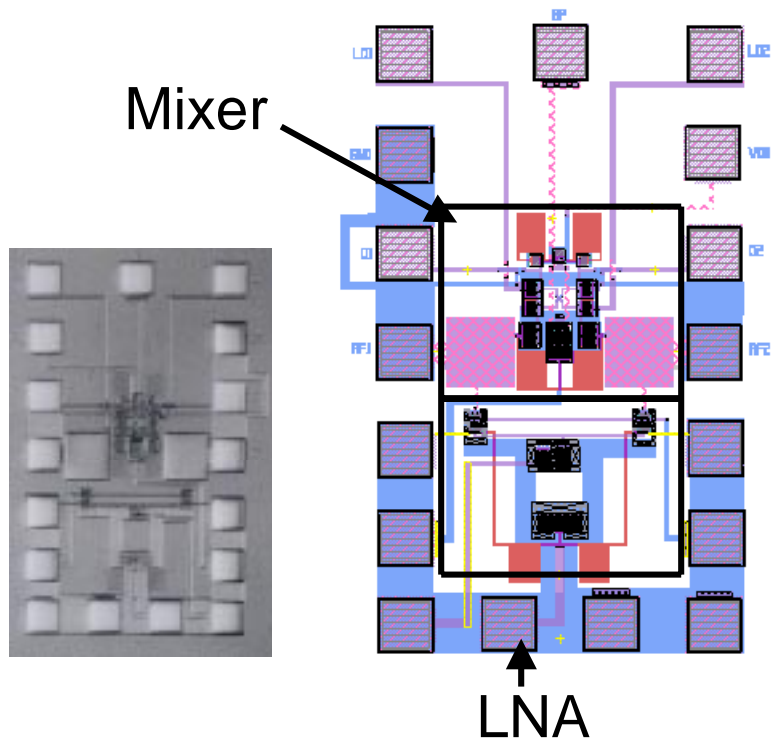- Multiple stage architecture, 0.8 μm technology




 - Single stage architecture, 0.6 μm technology




Gain/ Noise Measurements Single stage Architecture

1 kHz

 


Gain = 30 dB

 


Noise = 27 dB

50 kHz

 


Gain = 29.5 dB

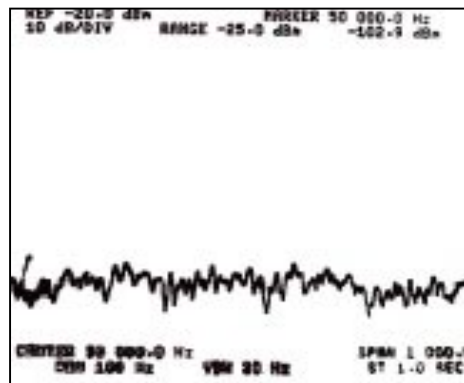


Noise = 17.5 dB

100 kHz

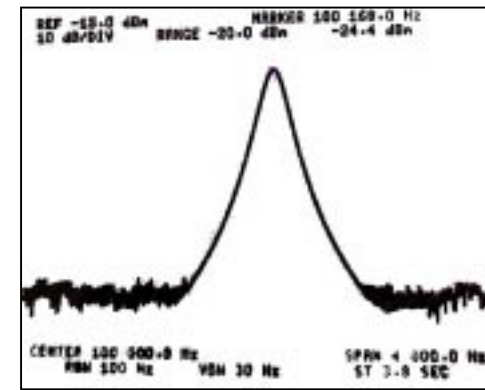


Gain = 29 dB

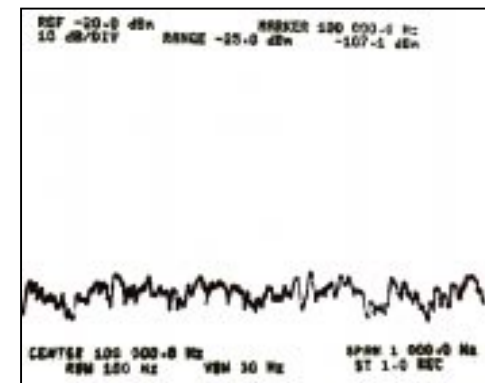


Noise = 16 dB

 Gain/ Noise/ 1dB Measurements Multi stage Front-end




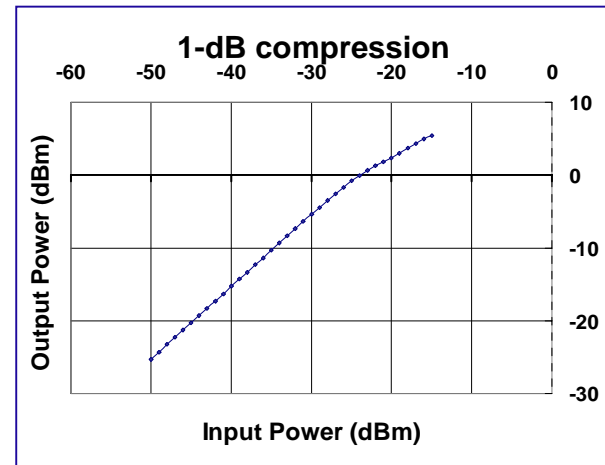1-dB compression
at -25dBm
(effective power)



LNA input = -43dBvrms
Mixer output = -17.85dBvrms
Gain = 25 dB

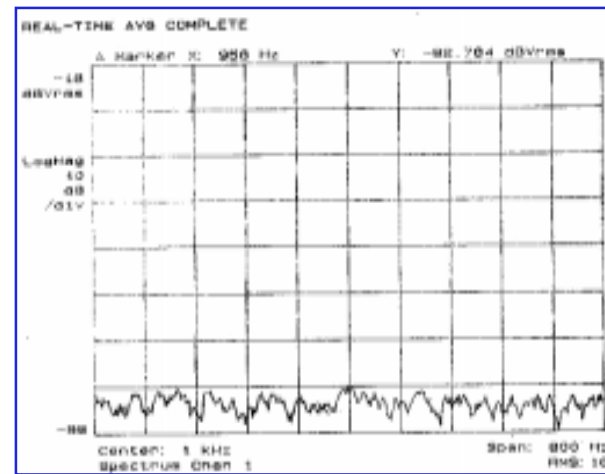This front-end:
At 1KHz: NF \approx 28dB
At 25KHz: NF \approx 19.5 dB



Comparing the results at 1kHz and 25 kHz


- Multi stage Architecture (0.8 μm)

	@1kHz	@25kHz
Gain	25 dB	24dB
Noise	26 dB	19.5dB
IP3	-15 dBm	-15 dBm
1dB	-25 dBm	-25 dBm

- Single stage Architecture (0.6 μm)

	@1kHz	@25kHz
Gain	30 dB	30dB
Noise	27 dB	21 dB
IP3	-13 dBm	-13 dBm
1dB	-23 dBm	-23 dBm


Final Results for Single Stage Front-end

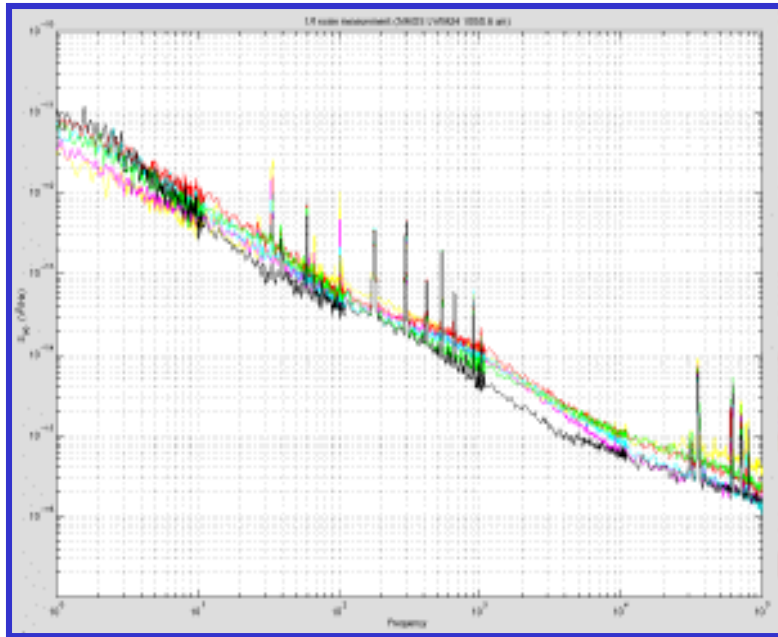

1/f S_{VG} measurement
(NMOS 100/0.6 μm)


	@ 100kHz
Gain	29 dB
Noise	16 dB
IP3	-13 dBm
1dB	-23 dBm

VCO Architecture

 

- HP CMOS 0.6 μm
- Cross-coupled PMOS transistors
 - isolated Nwell
 - less flicker noise
 - lower mobility
- Off-chip LTCC inductors
- MOSFET varactor tuning
- 3V, 150 μA
- -100 dBc/Hz @ 100 kHz
- 10 % tuning range

Micropower CMOS Quadrature VCO

 

Frequency Synthesizer Design

- Frequency synthesizer requirements:
 - switching time: less than 2 msec is adequate (depends on applications, usually latency tolerant)
 - frequency resolution: 250/500 kHz
 - low power operation: less than 1.5 mA drain current
- Frequency synthesizer techniques:
 - direct digital frequency synthesizer: fast switching, fine frequency resolution, but very high power (~1W, 12-bit, 100 MHz)
 - PLL: complex tradeoffs among frequency resolution, switching speed, and spurs; possible low power solution
- PLL architecture:
 - integer-N architecture (wide channel spacing and relaxed switching time requirements permit this low power PLL architecture)
- Design strategies:
 - high-Q LC-VCO: enables low power and low phase noise performance

Integer-N PLL


$$f_{ref} = f_{in}/R$$

$$f_{out} = N \cdot f_{ref}$$


$$N = (M+1)S + (P-S)M$$

$$= MP + S$$

$$f_{out} = (MP + S)f_{ref}$$

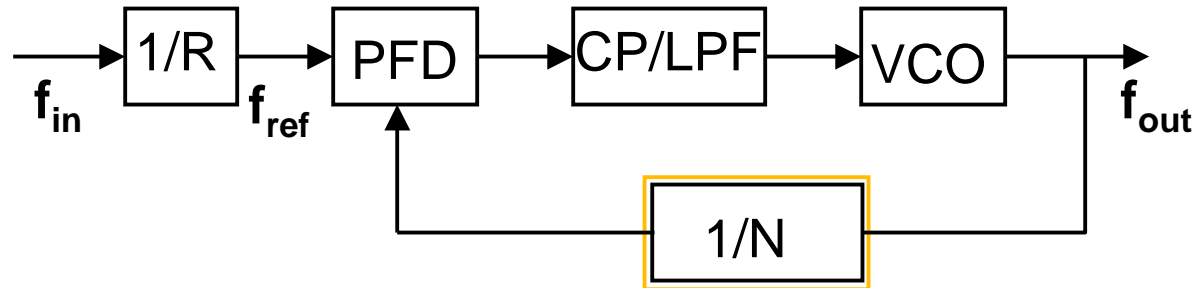

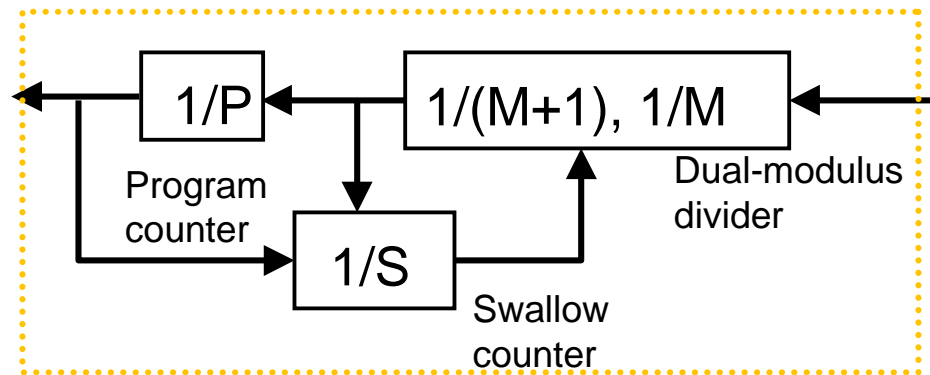
- To design lowpower:
- Wide channel spacing
- Relaxed switching time





$f_{ref}=250$ kHz, $f_{out}=902\sim 928$ MHz $\Rightarrow N=3609\sim 3711 \Rightarrow M=7, P=512, S=25\sim 127$

Dual-modulus divider (1/7, 1/8) is the most power hungry component (operated at near 1GHz) in the PLL.



Modified Integer-N PLL Architecture

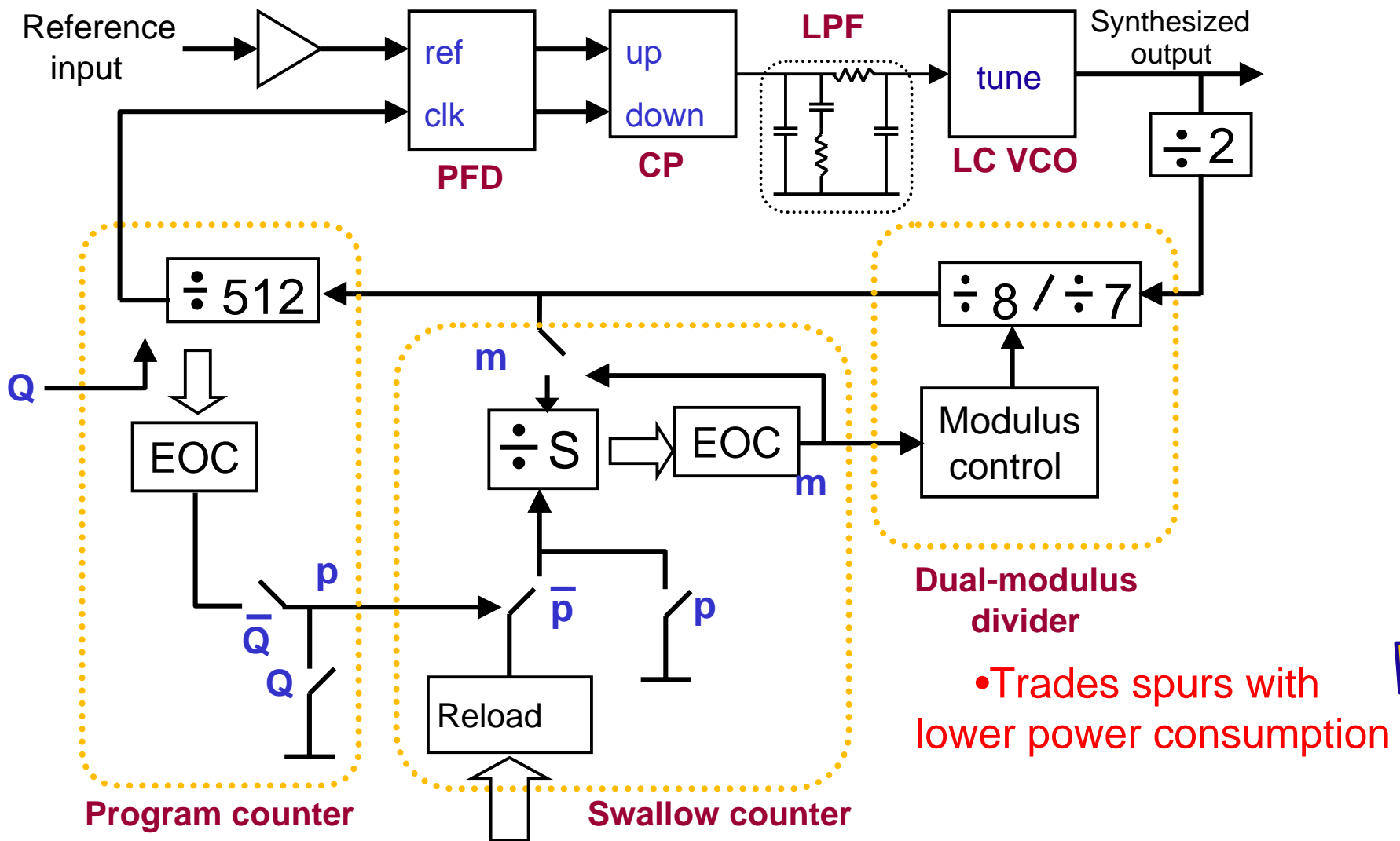

VCO Tuning

 
 


  - CMOS varactor : 20-30% of tuning range to compensate for process and temperature variation
- sensitive to noise at VCO tuning node




- Switched-capacitor provides coarse tuning
- CMOS varactor : fine tuning (much less tuning range is required in LC-VCO)
- less sensitive to noise

PLL with Coarse Tuning Loop

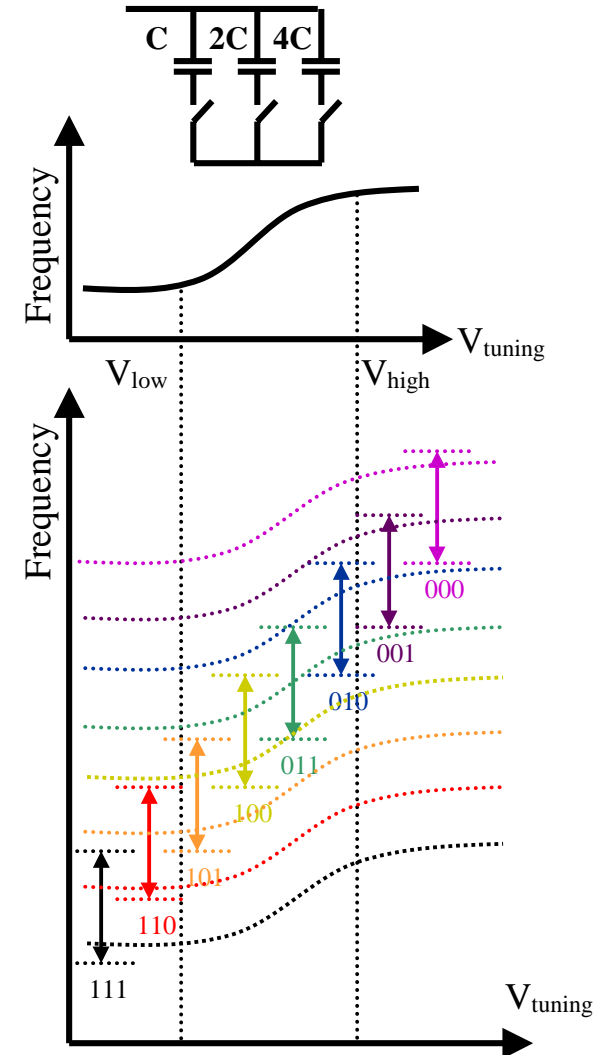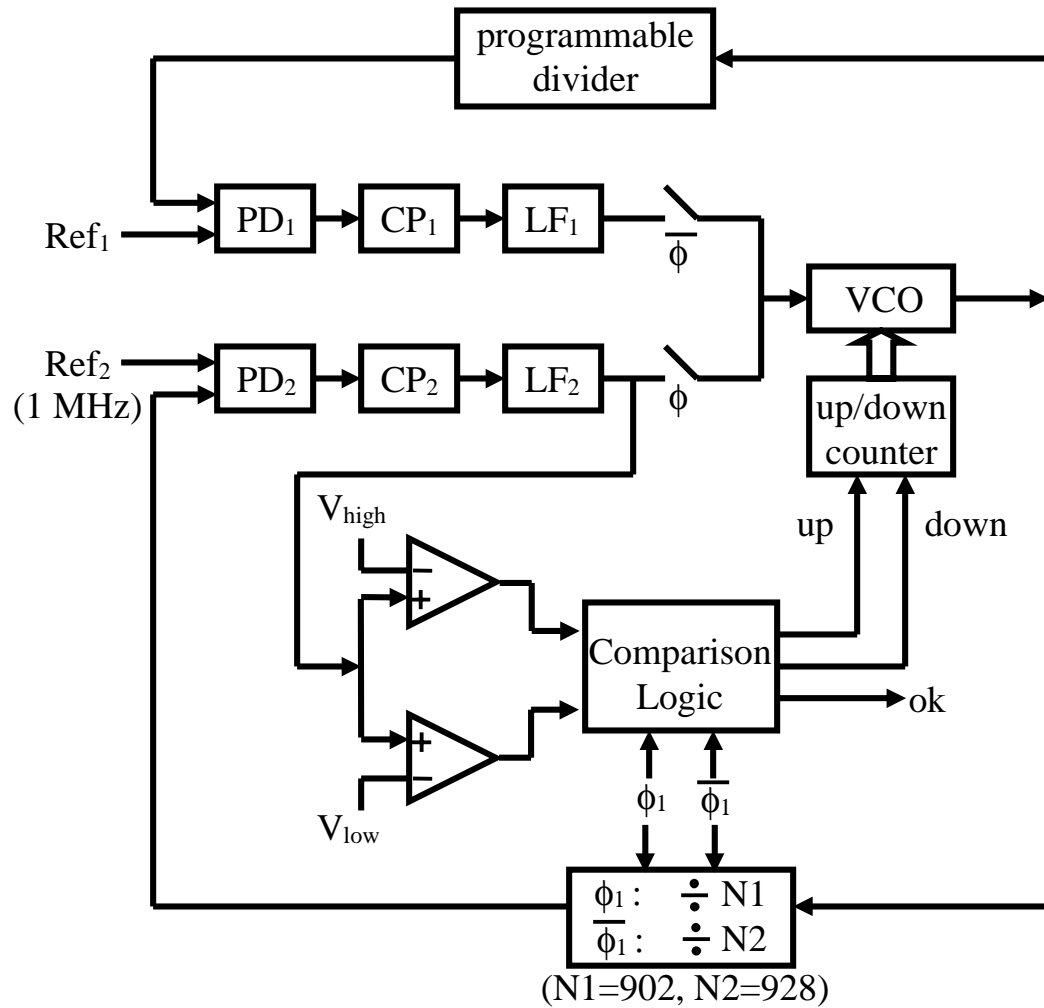


Layout

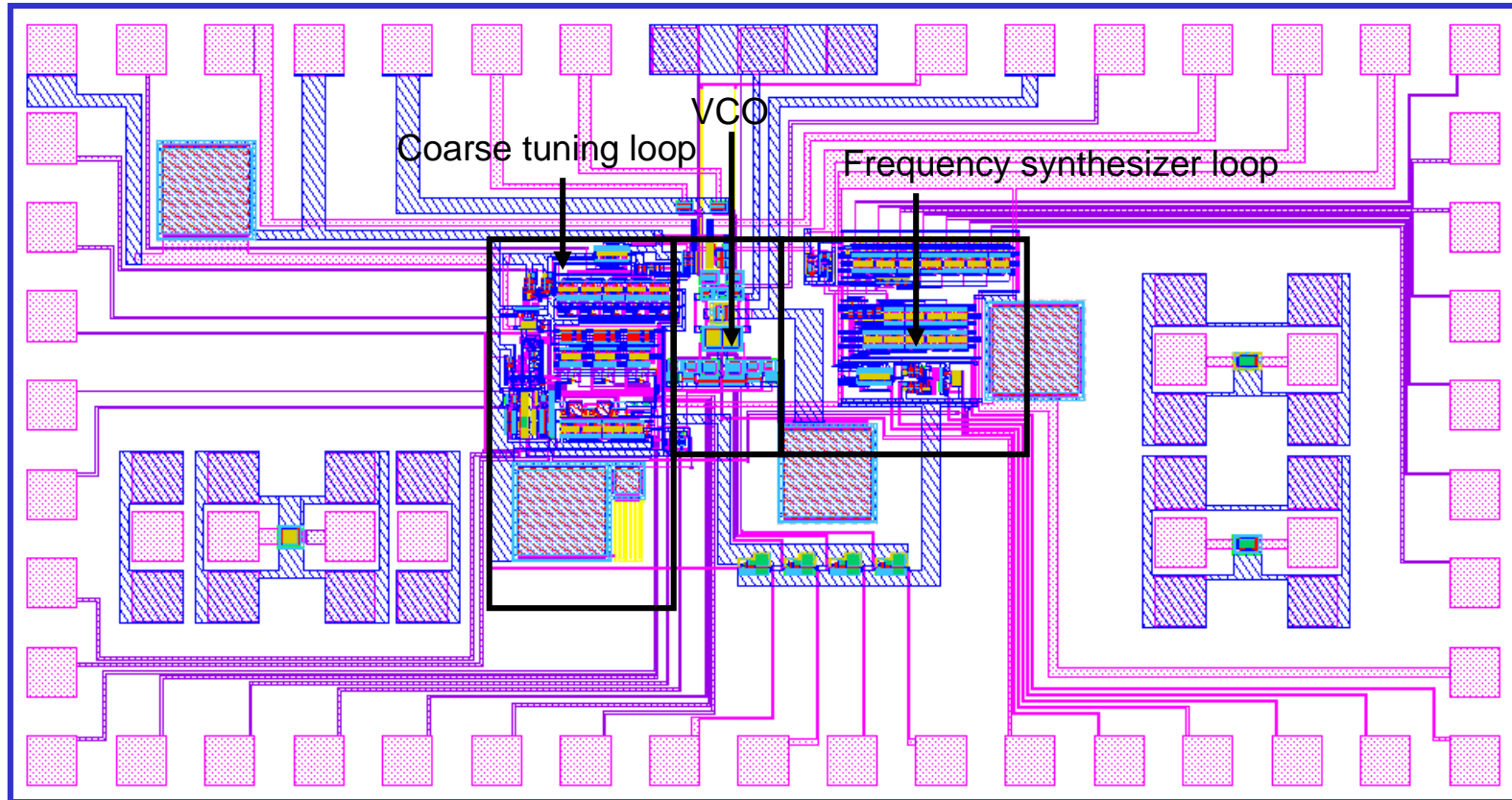

- HP 0.5um CMOS process
- Chip size: 2.6mm x 1.3mm

Transmitter Design

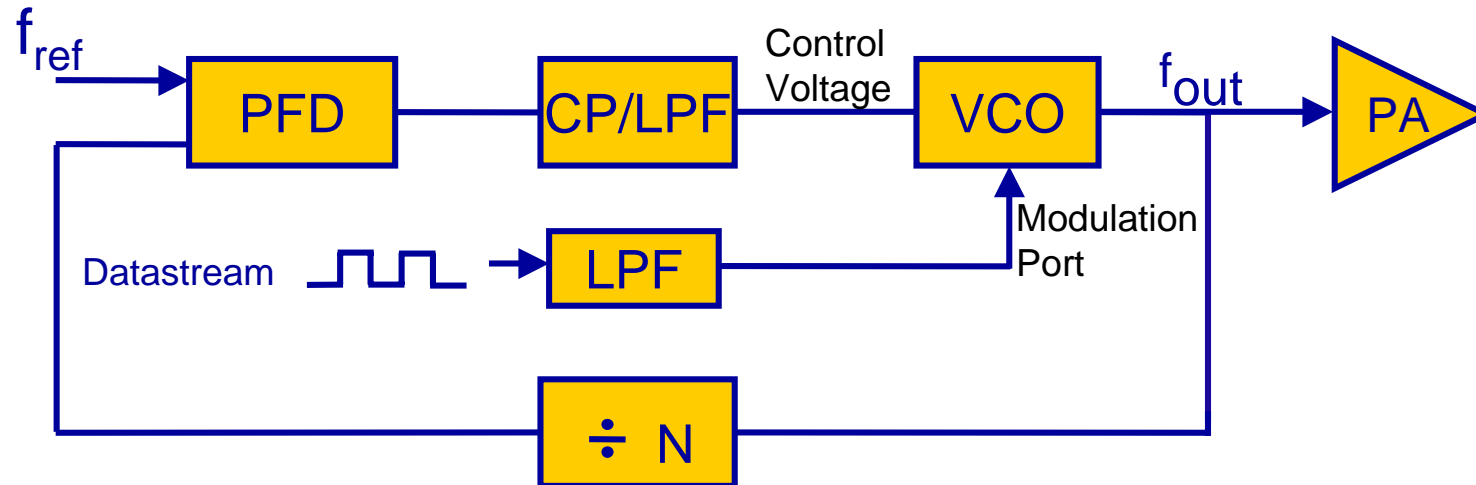



- Direct Modulation of VCO performed in Synthesizer Loop
- Loop bandwidth significantly less than frequency of modulation signal applied to VCO
- Mixerless design reduces power consumption
- Resistance to Injection Locking

Power Amplifier Design


- Goal: To achieve low output power with high efficiency
- FSK system allows for use of non-linear power amplifier resulting in greater efficiency
- Variable output power desirable in order to deliver required signal strength at receiver, leading to overall system efficiency
- Efficiency is difficult to maintain over variable power range
- Power dissipation of predriver is increasingly important as desired output power decreases
- Variable PA with output powers ranging from 7mW to .5mW with efficiencies of 43% to 10% currently under development

PA Circuit

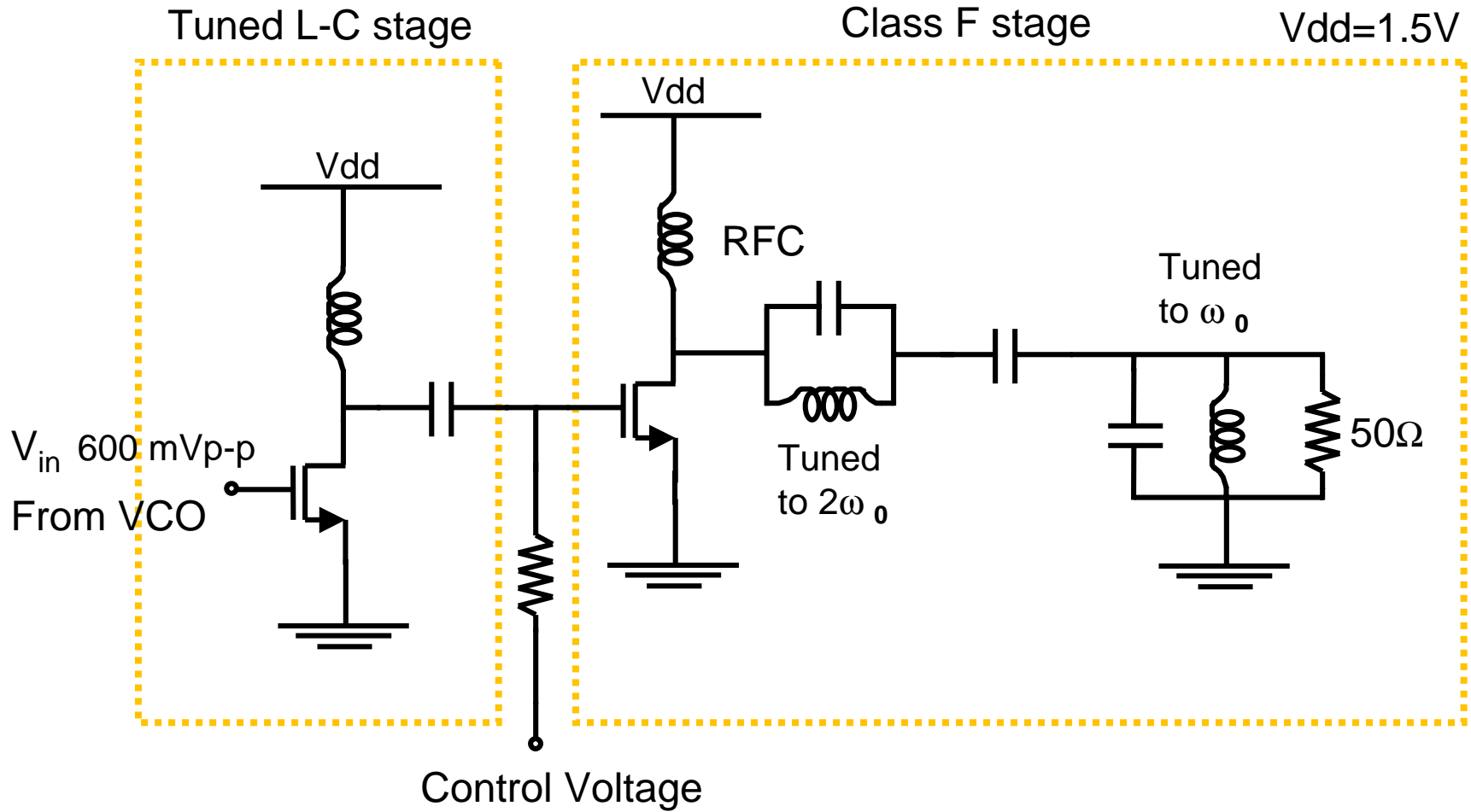

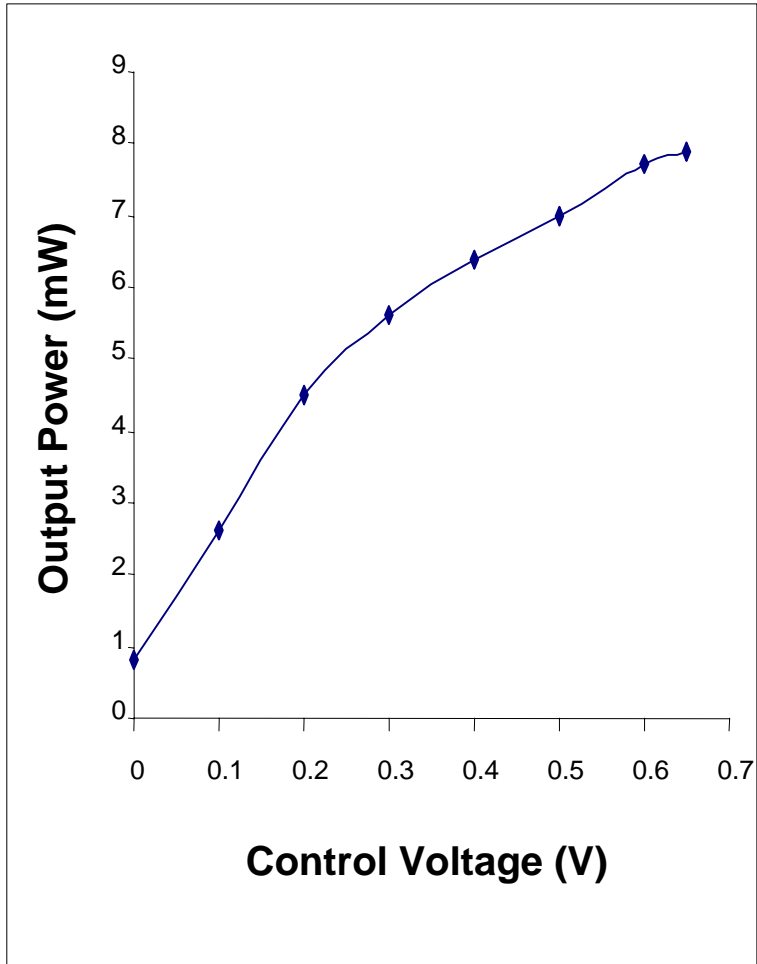

Output Power vs. Control Voltage



 


Efficiency vs. Output Power

WINS integration

- Low Temperature Co-fired Ceramic
   
$$L = 20\text{nH } Q \approx 20 @ 1\text{GHz}$$



Summary

- WINS project RF components trade off sensitivity for greatly reduced power consumption
- A front-end receiver with a total current consumption of 140 μA has been developed and tested in 0.6 μm CMOS technology
- The front-end includes a preselector which provides gain and filtering before the LNA
- The receiver has: Gain = 30dB, NF = 16dB, 1-dB compression = -23dBm

Acknowledgment

- DARPA
- Scrantom Engineering, Inc. (SEI)
- Ms. M.Rofougaran, Dr. D. Pelhke