


Embedded Systems

Ch 13A
**Analog Interface &
Codec**



Byung Kook Kim

Dept of EECS

Korea Advanced Institute of Science and Technology

Overview

- 1. *Introduction*
- 2. *A/D Conversion*
- 3. *ADC Interface*
- 4. *Sensor Interface*
- 5. *D/A Conversion*
- 6. *PWM*

- *References*
 - *Steve Heath, "Embedded Systems Design", 2nd Ed., Newnes, 2003.*

1. Introduction

- How to sample external voltages and convert them into digital values
 - Sources
 - Sensors
 - Convert physical quantity into electrical quantity
 - Represent light levels, temperature, vibration
 - Analog signals
 - Output of microphone or audio system
 - Conversion
 - Analog-to-digital converter
- How to turn digital data into an analog output voltage
 - Destinations
 - Speaker, motor
 - Conversion
 - Digital-to-analog converter

A 3D, isometric logo for ADC (Analog-to-Digital Converter). The letters 'A', 'D', and 'C' are rendered in a bold, sans-serif font. The 'A' is orange, the 'D' is yellow, and the 'C' is orange. They are arranged in a slightly overlapping, perspective view.A 3D, isometric logo for DAC (Digital-to-Analog Converter). The letters 'D', 'A', and 'C' are rendered in a bold, sans-serif font. The 'D' is purple, the 'A' is blue, and the 'C' is purple. They are arranged in a slightly overlapping, perspective view.

2. A/D Conversion

■ Amplifier

- Increases a given input voltage
 - Ex: Sensor output amplification from 5mVpp to 5Vpp
$$\text{Gain} = V_{\text{out}} / V_{\text{in}} = 1000$$
- Implementation
 - Using vacuum tubes, transistors, or OP amps
 - Inverting amplifier
 - Non-inverting amplifier
 - Differential amplifier
 - Restrictions
 - Frequency response
 - Home stereo: 20 Hz – 20 kHz
 - Sensor: flat (ideally)
 - Distortion
 - Total Harmonic Distortion (THD) in audio amp.

A/D Conversion (II)

■ Analog-to-Digital converter (ADC)

- A device that converts an analog input voltage to a digital number
- Coder part of codec (Coder-DECoder)
- Used in maaaaaany areas
 - Microphone in PC
 - CD mastering
 - DVD mastering
 - Sensor processing
- Types
 - Integrating ADC: Counter, DAC, Comparator. $2^{(n-1)}$ clocks average.
 - Successive-approximation ADC: Binary search. n clocks.
 - Flash ADC (parallel ADC): $(2^n - 1)$ comparators, encoding logic.

A/D Conversion (III)

■ Sampling


- Sample rate: samples per second
 - $>2x$ signal bandwidth to avoid aliasing: Nyquist sampling theory
 - Faster: expensive ADC required

■ Quantization

- Accuracy of each sample (resolution)
- Number of bits in digital data
- Quantization level: $\text{Full_scale_voltage} / (2^n)$
 - 8-bit ADC: $1/256$
 - 12-bit ADC: $1/4096$
 - 16-bit ADC: $1/65536$. More expensive
 - Ex: Temperature sensor with a range 0 to 100 deg.C, 0.5 deg. Resolution: 8-bit ADC is sufficient.
 - Ex2: CD - 16-bit, 44.1 kHz, stereo. 600 MB/h.

■ Conversion equation

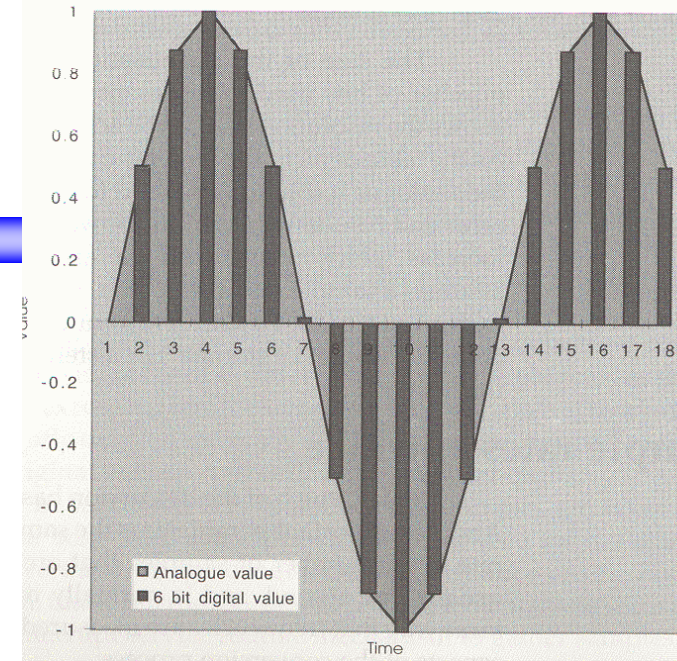- Analog signal = (digital sample / max value) * reference voltage.



3. ADC Interface

■ Wide range of ADCs

- Low-cost, low-speed ADCs: Simple voltage conversion
- High-speed, precise (and expensive) ADCs: Sampling video streams
- Built-in ADCs in microcontrollers: Simple interface

■ Considerations

- Number of bits (resolution): 8/12/14/16
- Conversion rate (speed)
- Interface: Parallel, serial, SPI, I2C
- Analog multiplexer, Sample-and-hold: Internal or external
- Package
- Cost


ADC Interface (II)

■ Maxim MAX1245

- A good general-purpose ADC for sensor applications
 - 8 channels of analog input
 - 100K samples/sec
 - 12-bit resolution
 - Internal track-and-hold
 - Interface: SPI, microwire, serial (TI DSP)
 - DOUT: MISO, DI: MOSI, SCLK: SCLK
- Operation
 - Start command to ADC via the SPI interface
 - Specifies the channel and other ADC settings
 - Internal/external clocks
 - SPI SCLK can be used as ADC clock

ADC Interface (III)

- MAX1245 Interface ->

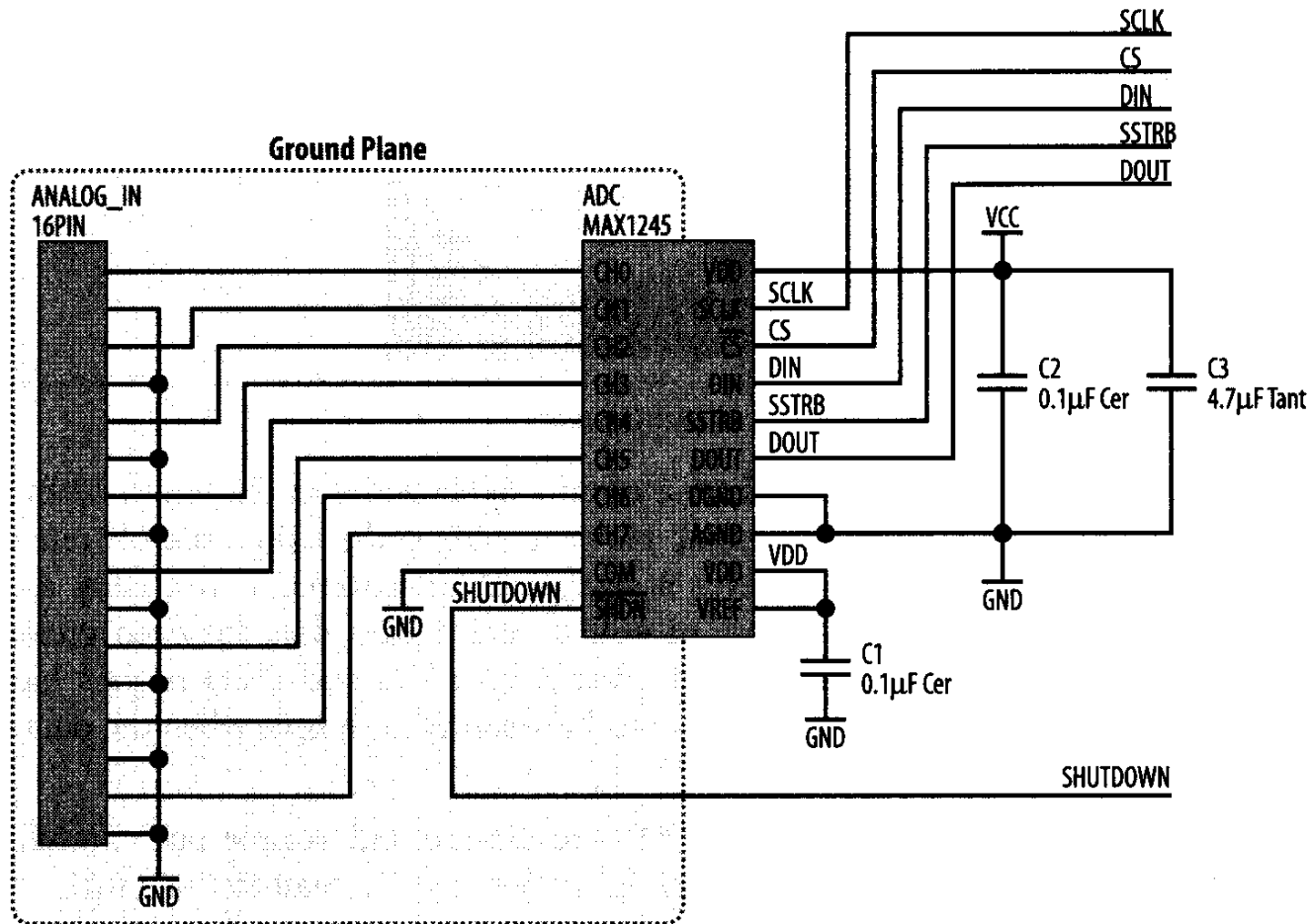

ADC Interface (IV)

- MAX1245
 - Ability to enter low-power mode
 - Hardware: SHDN' pin. Low: low-power operation
 - Also specifies the clock frequency (1: 1.5 MHz, 0: 225 kHz)
 - Software:
 - If the two least-significant bits of the start command are both 0, then the MAX1245 is placed in shutdown.
 - Conversion and shutdown possible: Conversion and then shut-down.
- Power
 - In the range 2.7V to 3.3V
- Grounds
 - COM: Ground reference for analog inputs
 - DGND: ground for digital section
 - AGND: ground for analog section
 - -> Connected together at a single point near AGND.

4. Sensor Interface


■ A. Temperature Sensor

■ Applications

- Room temperature: heating & cooling systems
- Temperature recorder: shipment of fruits, vegetables, frozen foods, and flowers

■ AD22100/22103 temperature sensors by Analog Devices

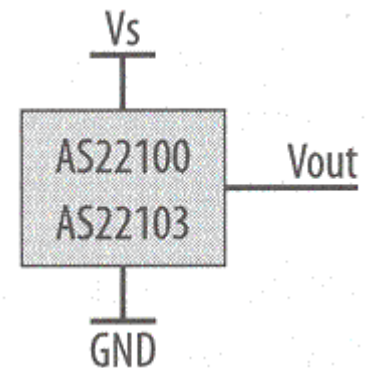
- Easy to use
- 3-pin device: power, GND, and Vout ->
- 5V (AD22100), 3.3V (AD22103)



Sensor Interface (II)

- *Temperature sensor (Cont'd)*
 - AD22100/22103
 - Temperature range: -50 deg.C to 150 deg.C
 - 22.5 mV/deg.C for AD22100
 - $V_{out} = (V_s/5) * (1.375 + 0.0225 * T_A)$
 - $T_A = (((V_{out} * 5) / V_s) - 1.375) / 0.0225$
 - 28 mV/deg.C for AD22103
 - $V_{out} = (V_s/3.3) * (0.25 + 0.028 * T_A)$
 - $T_A = (((V_{out} * 3.3) / V_s) / 0.028)$



- Interfacing ->

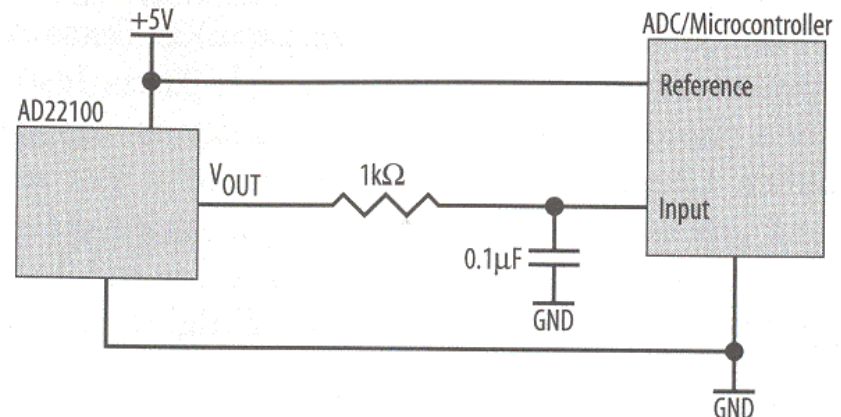

Sensor Interface (III)


■ B. Light Sensor

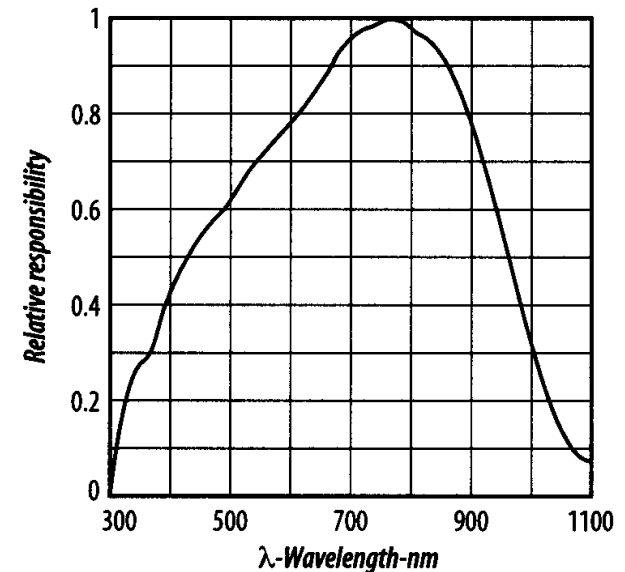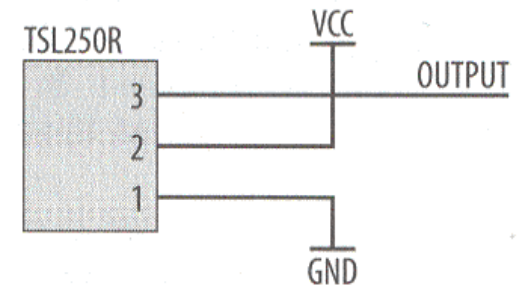- Applications
 - Artificial lighting systems
 - Security detector: Checks light interruption
- TAOS TSL250R
 - Texas Advanced Optical Solutions Inc.
<http://www.taosinc.com>
 - Consists of a photodiode and an integrated amplifier
 - Simple 3-pin device:
 - Vcc, GND, Output ->
 - Spectral response ->
 - Supply voltage between 2.7V to 5.5V
 - Consumes typically only 1.1 mA
 - Output: 0 to 4V



Sensor Interface (IV)

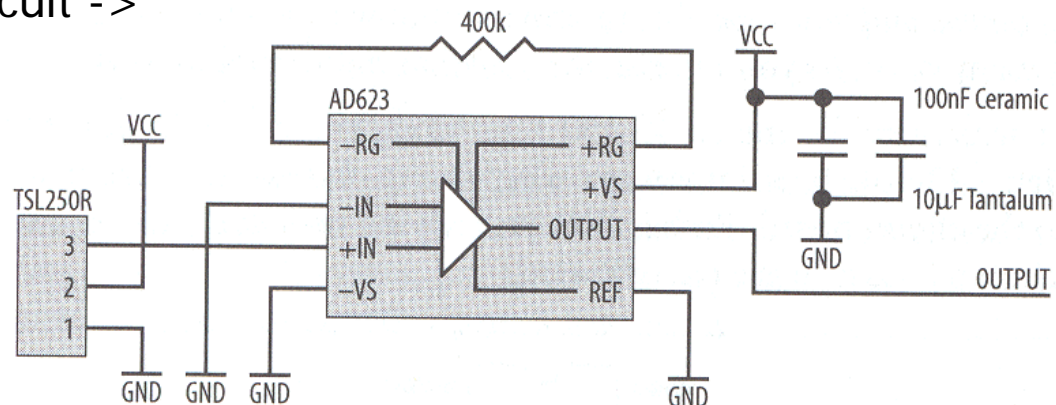- *Light sensor (Cont'd)*
 - Amplifying the light sensor
 - 4V to 5V. Gain: 1.25
 - AD623: A good general-purpose op amp
 - Rail-to-rail operation, Single supply voltage
 - Requires very little current, Easy to use
 - Single external resistor to set gain
 - $R_G = 100 \text{ kohm} / (\text{Gain} - 1)$
 - 1% accurate R req'd
 - Amplifier circuit ->




Sensor Interface (V)

■ C. Accelerometer


- ADXL150 (Analog Devices)
 - Single-axis (one-dimensional) accelerometer
 - Resolution 10 mg ($1 \text{ g} = 9.8 \text{ m/s}^2$)
 - Full-scale range $\pm 50\text{g}$
- ADXL250
 - Dual-axis (two-dimensional) accelerometer
- Applications
 - Measure linear acceleration of vehicles
 - Gentle vibrations and shifts
 - Seismometer
 - Vibrations of ground shift in mines, in tunnels, or at building sites
 - Monitor motion.

Sensor Interface (VI)

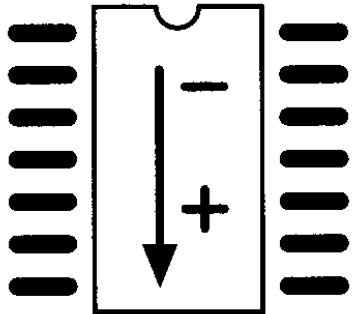

■ Accelerometer (Cont'd)

- Axis of sensitivity for ADXL150 ->
 - Use strong glue under the chip
- ADXL150 circuit ->
 - No external components except power supply
 - Incorporates sensor, signal conditioning, and amplification
 - Output directly interfaced to an ADC
 - TESTPOINT: Used during manufacturing process
 - Power supply 4 – 6 V (5 V exact desirable)
 - $V_{out} = V_s/2 - (\text{sensitivity} * V_s/5 * \text{acceleration})$
 - Sensitivity: 33.0 to 43.0 (38.0 nominal) for range +/-50g
 - Sensitivity doubling
 - Connect output to the OFFSET_NULL pin (+/-25g)
 - SELF-TEST: Verify correct operation (artificial force)

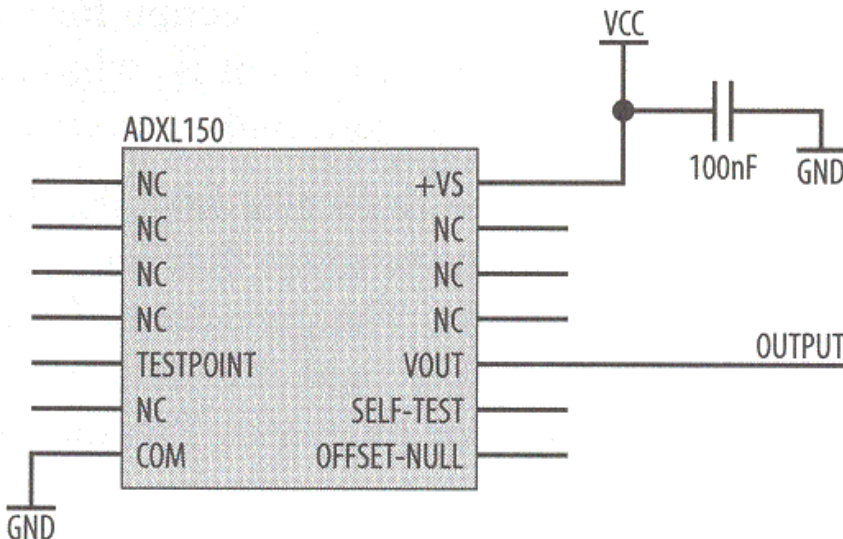

Sensor Interface (VI)

■ D. Pressure sensors

■ Applications

- Air pressure for weather monitoring and prediction
- Cars: manifold pressure
- Washing machine: water level
- Biomedical: blood pressure
- Measure altitude (air pressure dep. on height above sea level)
- Ocean depth

■ Sensing methods


- Deflection of a diaphragm separating two chambers
 - Absolute, differential, gauge (wrt atmosphere)

Sensor Interface (VIII)

■ *Pressure sensors (II)*

■ **Motorola MPXA6115A**

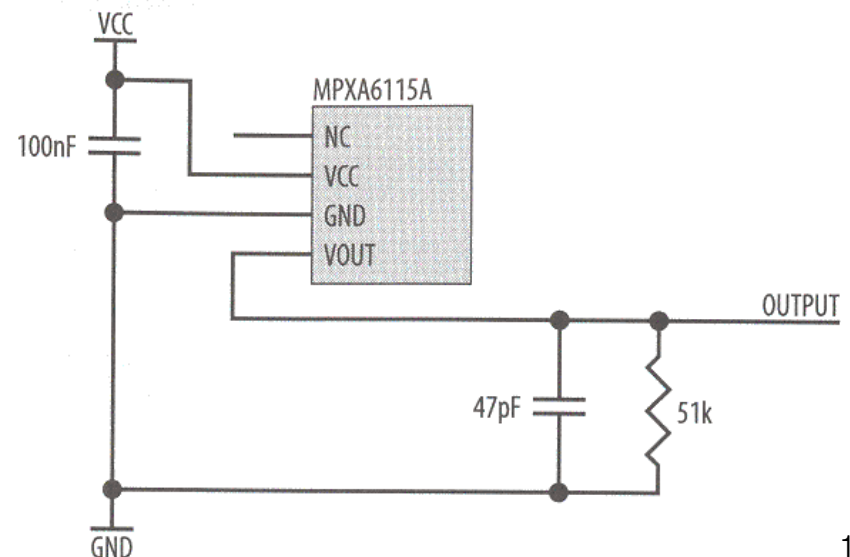- Absolute pressure sensor ->
- 5 V supply
- Output voltage 0.2V to 4.8V (15kPa to 115kPa)
- Integrates signal conditioning, temperature compensation
- Requires
 - External power supply and decoupling capacitor only
 - RC filter at the output




Sensor Interface (IX)

- *Pressure sensors (III)*

- **KP100 by Infineon**

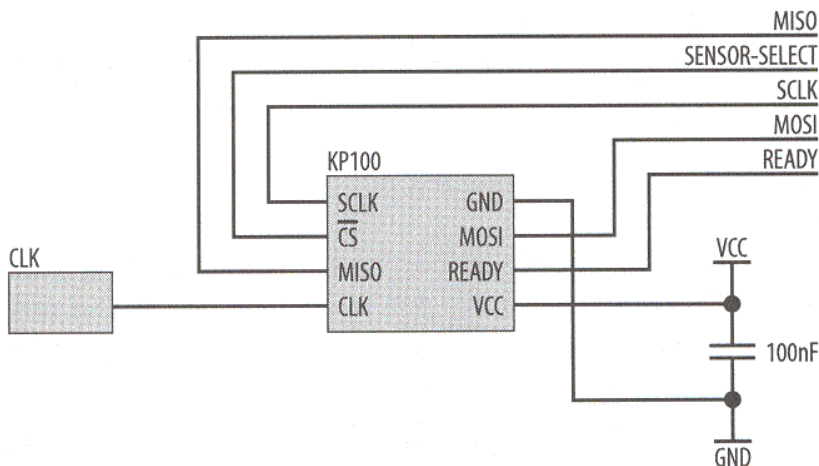- Absolute pressure sensor
- Incorporates a built-in ADC
- Much less susceptible to noise and interference
- SPI interface ->
- 5V supply and decoupling capacitor
- READY output: may interrupt the processor
- Separate CLK input: 4MHz or 8MHz




Sensor Interface (X)

■ E. Magnetic field sensor

■ AD22151 by Analog Devices

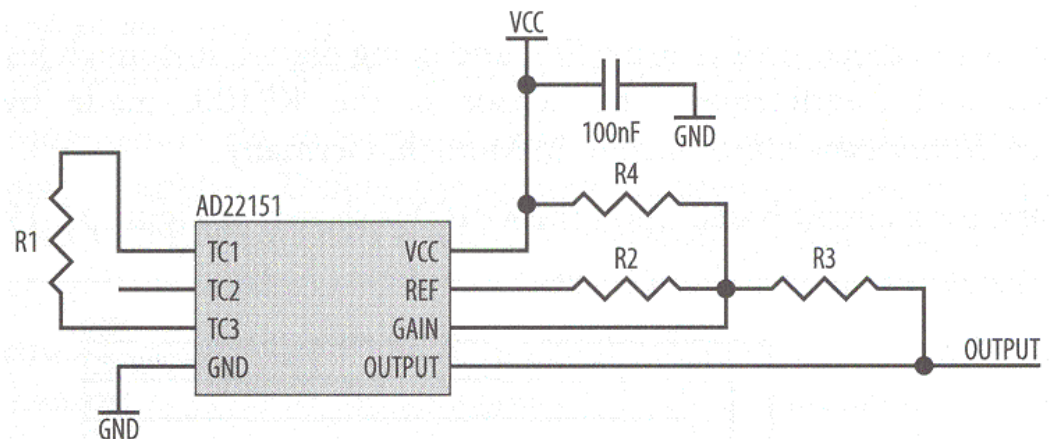
- Measure position and proximity
 - Magnetic source as a reference point
- Built-in temperature compensation and amplification
- Sensor circuit ->
 - R1: Temperature compensation resistor
 - R2, R3: Gain
 - R4: Voltage offset



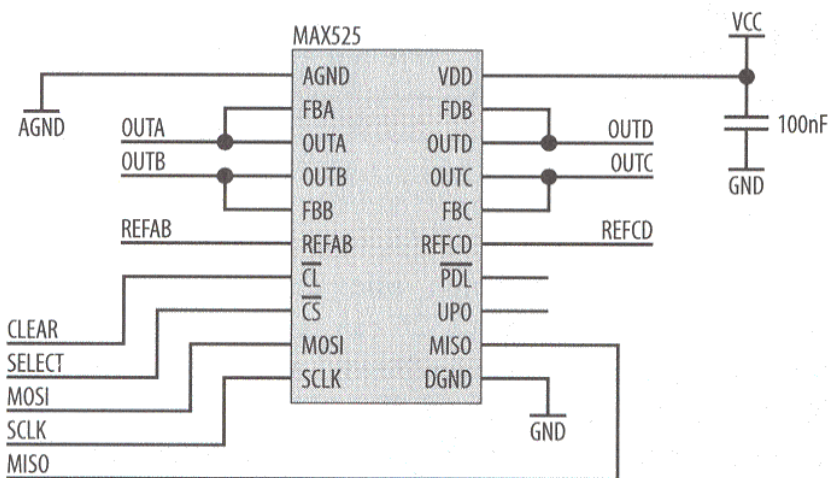5. D/A Conversion

■ Digital-Analog Converter


- Take digital data and convert it into an analog signal
- Digital input
 - Bus, SPI, or I²C
- **MAX525 by Maxim**
 - 12bit DAC with SPI interface ->
 - 4 channels of analog output
 - OUTA, OUTB, OUTC, OUTD
 - Output amplifiers on-chip
 - Feedback inputs: FBA, FBB, FBC, FBD
 - Voltage reference inputs: REFAB, REFCD
 - At least 1.4V or more below VCC
 - Output voltage
 - $V_{out} = (V_{ref} * code / 4096) * gain$



D/A Conversion (II)

- *MAX525 (Cont'd)*


- Daisy chaining multiple MAX525s ->

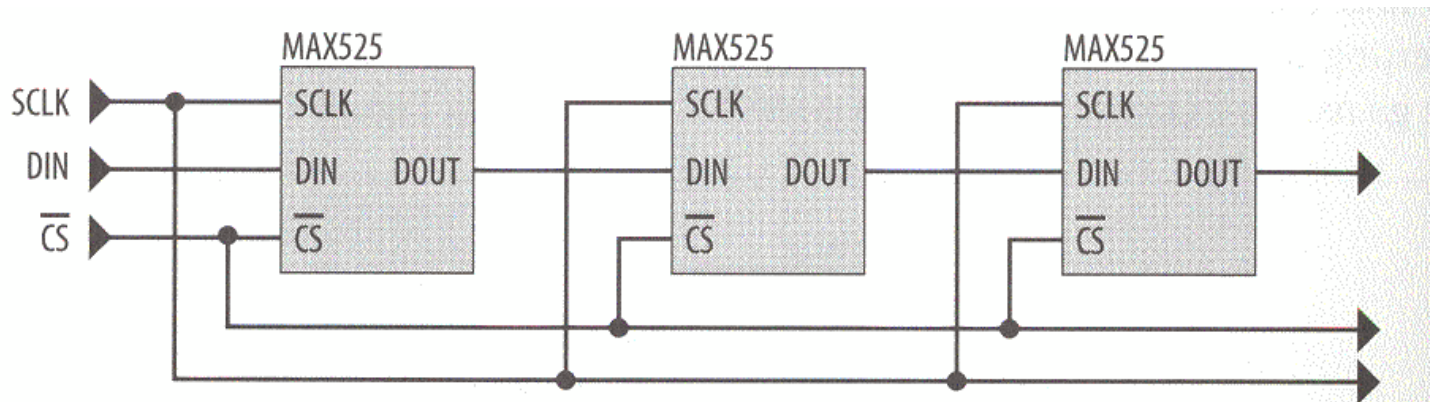


- CLb input: All outputs to lowest value
- Low-power mode under software control
- PDLb input: power-down lockout
- UPO: User Programmable Output
 - General-purpose

D/A Conversion (III)

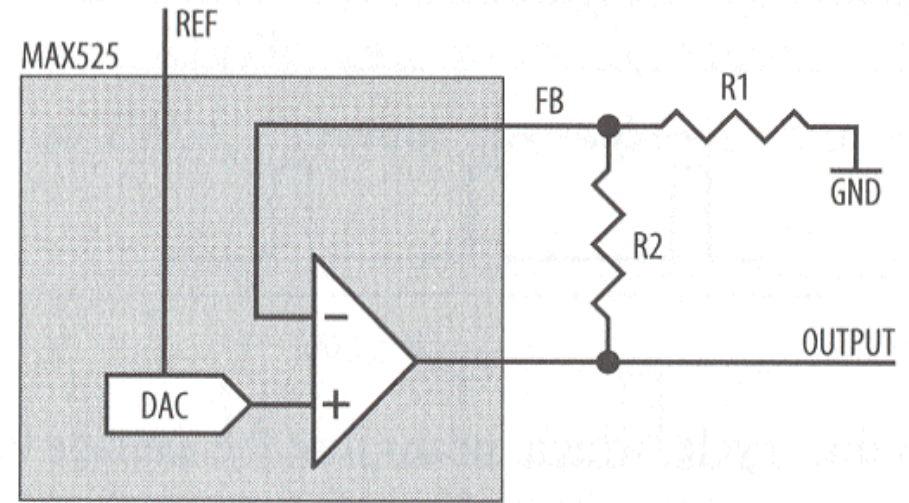- *MAX525 (Cont'd too)*
 - Nonunity gain amplifier ->
 - Gain = $1 + R2 / R1$



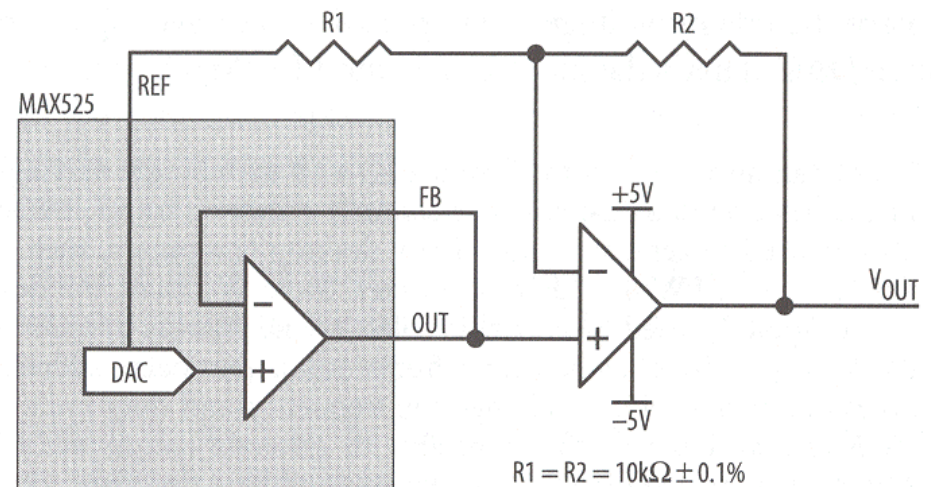- Bipolar output
 - Use external amplifier with bipolar supplies ->



6 PWM

■ Pulse Width Modulation

- Use one digital output to generate analog output
 - Use a constant frequency (or period)
 - Change the duty cycle
 - Average value of the output is proportional to the duty cycle
- Low-pass filter
 - Averaging
 - Convert the pulse to an analog voltage
- Applications
 - Drive LEDs
 - Drive a speaker
 - Frequency and duty -> pitch and volume


PWM (II)

- Motor Control: DC motor drive

- DAC + linear amplifier
 - Poor low-speed operation
 - Low power efficiency
- PWM + switching amplifier
 - Better low-speed operation
 - High power efficiency

H-bridge ->

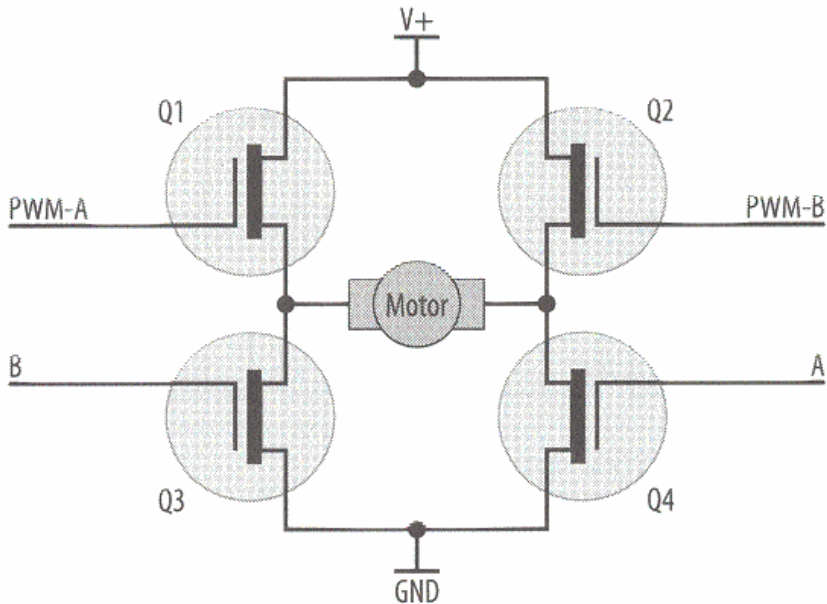- Bidirectional drive with single power supply
- Q1, Q3 simultaneous ON: short circuit!



PWM (III)

- MC33186 by Motorola ->

- More functionality
- Easier to control
- V+: 5 to 28V
- TTL compatible inputs
- Switch continuous current up to 5A
- Built-in short-circuit and over-current protection

- Pins

- CP: Charge pump
- Forward: DI1=0, DI2=1, IN1=1, IN2=0
- Backward: DI1=0, DI2=1, IN1=0, IN2=1
- Freewheeling: DI1=0, DI2=1, IN1=IN2
- Disabled: DI1=1 or DI2=0
- SF output: Status Flag.

